

## Example 9-2

In Example 9-1, find the voltage regulation of the transformer.

### Example 9-1

A single-phase transformer has the following specifications:

20 kVA, 2400/240V, 60 Hz, full load at power factor of 0.8 lagging,  $R_p = 0.8 \Omega$ ,  $X_p = 3 \Omega$ ,  $R_s = 0.008 \Omega$ , and  $X_s = 0.03 \Omega$ .

- Find the equivalent circuit parameters referred to primary. Draw the equivalent circuit diagram and phasor diagram referred to primary.
- Find  $\bar{V}_p$ .

Equivalent circuit was referred to the primary side.

$$VR = \frac{V_p - aV_s}{aV_s} \times 100\%$$

$$a\vec{V}_s = 2400 \angle 0^\circ \text{ V} \quad \rightarrow \quad aV_s = 2400 \text{ V}$$

$$\vec{V}_p = 2440.86 \angle 0.75^\circ \quad \rightarrow \quad V_p = 2440.86 \text{ V}$$

$$\therefore VR = \frac{2440.86 - 2400}{2400} \times 100\% = \boxed{1.70\%}$$